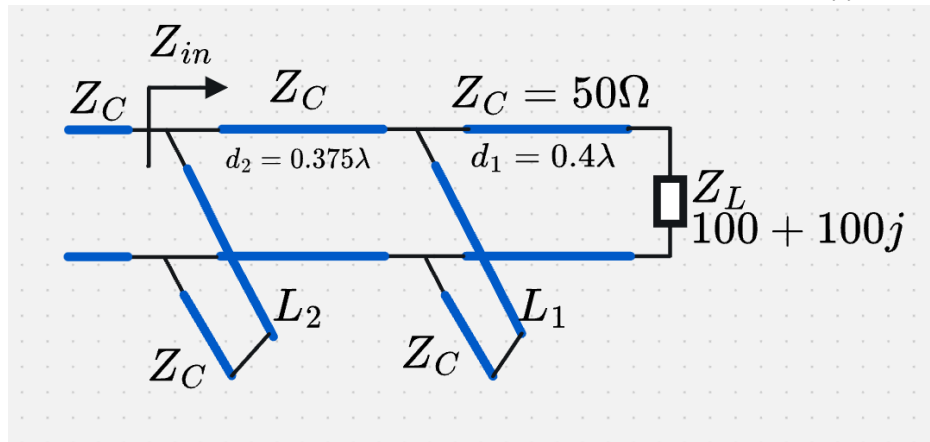


## Two Stubs Example

in this example we will find  $L_1$  and  $L_2$  that our load will be matched with  $Z_{in}$ .



Solution Steps:

1. Normalize the load impedance,  $\bar{Z}_L = Z_L/Z_C$ . We will drop the bar notation from now on.
2. Plot the normalized load on the smith chart. The real part lies on the circles and the imaginary on the arcs. Their intersection is our load.
3. Draw a circle from the origin of the smith chart with  $Z_L$  as its radius.
4. Rotate the load a distance of  $d_1$  towards the generator. Rotation towards the generator is done by inserting  $d_1 < 0$  and it rotates  $Z_L$  clockwise.
5. Since we are dealing with a parallel connection working with admittance is easier. For that mirror the impedance by 180 degrees to get  $Y_{L,rot}$ .
6. Go along the circle for  $Y_{L,rot}$  until you hit the real axis, mark this point as A.
7. The point on the right edge of the real axis represents a short circuit, mark this point as B. from the middle point between A and B, draw a circle with radius  $0.5(B - A)$ . As a sanity check the points A,B and  $Y_{L,rot}$  should be on that circle.
8. Locate the unity circle of  $1 + Aj$  and rotate it a distance  $d_2$  towards the load, rotation towards the load is counter clockwise. This is done by inserting  $d_2 > 0$ . Mark the two intersection points of the circles as  $Y_{int1}$  and  $Y_{int2}$ .
9. Calculate the difference  $Y_{dif} = Y_{L,rot} - Y_{int}$ . Since they are on the same circle the result should be purely imaginary.
10. Find the location of  $Y_{dif}$  and calculate its arc length from point B, that lies on the right edge of the chart, that is the value for  $L_1$
11. Rotate the unity circle of  $1 + Xj$  with the points  $Y_{int}$  back to its original place. The negative of the imaginary value of  $Y_{int}$  is the value of the admittance.
12. Same as step 10.

## Steps One, Two and Three

Step one: normalize the load

$$\bar{Z}_L = \frac{Z_L}{Z_C} = \frac{100 + 100j}{50} = 2 + 2j$$

Step two and three:

Plot  $\bar{Z}_L$  and a circle around the origin with  $\bar{Z}_L$  as its radius.

tk

0. Open a New Chart

☒ Short Circuit Mode ☒ Z Mode

1. Enter Load Impedance ( $Z = R + jX$ ):

R:  X:

2. Enter Rotation Distance:

d1:

3. Mirror  $\Gamma$ :

4. Enter the distance between the stubs:

d2 > 0:


5. Subtract For L1:


6. Rotate Unity Back:

7. Clear a Point:

8. Clear a Circle:

9. Clear an Arc:

  $Z_L : (2+2j)$

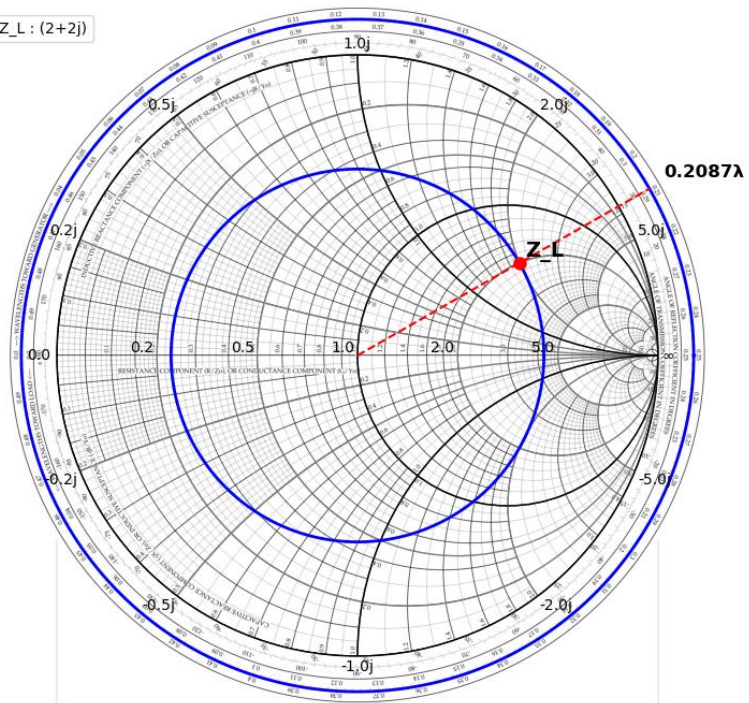

## Step Four

Step four:

Rotate the load a distance of  $d_1 < 0$  towards the generator.

tk

0. Open a New Chart

☒ Short Circuit Mode ☒ Z Mode

1. Enter Load Impedance ( $Z = R + jX$ ):  
R:  X:

2. Enter Rotation Distance:  
d1:

3. Mirror  $\Gamma$ :

4. Enter the distance between the stubs:  
d2 > 0:


5. Subtract For L1:

6. Rotate Unity Back:

7. Clear a Point:

8. Clear a Circle:

9. Clear an Arc:

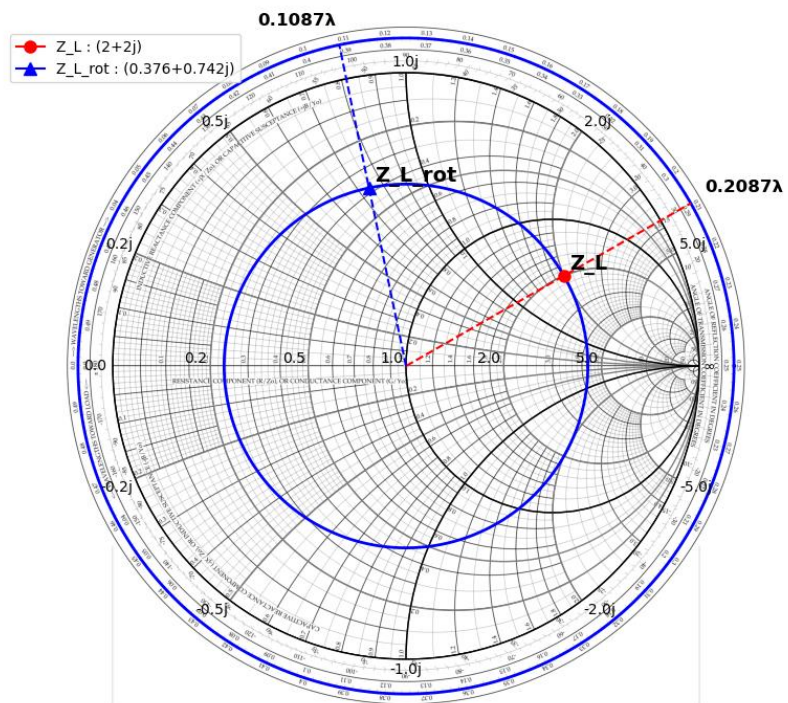

## Step Five

Step four:

Mirror the impedance to get admittance.

TK

**0. Open a New Chart**

☒ Short Circuit Mode ☐ Z Mode

**1. Enter Load Impedance ( $Z = R + jX$ ):**

R:  X:

**2. Enter Rotation Distance:**

d1:

**3. Mirror  $\Gamma$ :**

**4. Enter the distance between the stubs:**

d2 > 0:


**5. Subtract For L1:**

**6. Rotate Unity Back:**

**7. Clear a Point:**

**8. Clear a Circle:**


**9. Clear an Arc:**

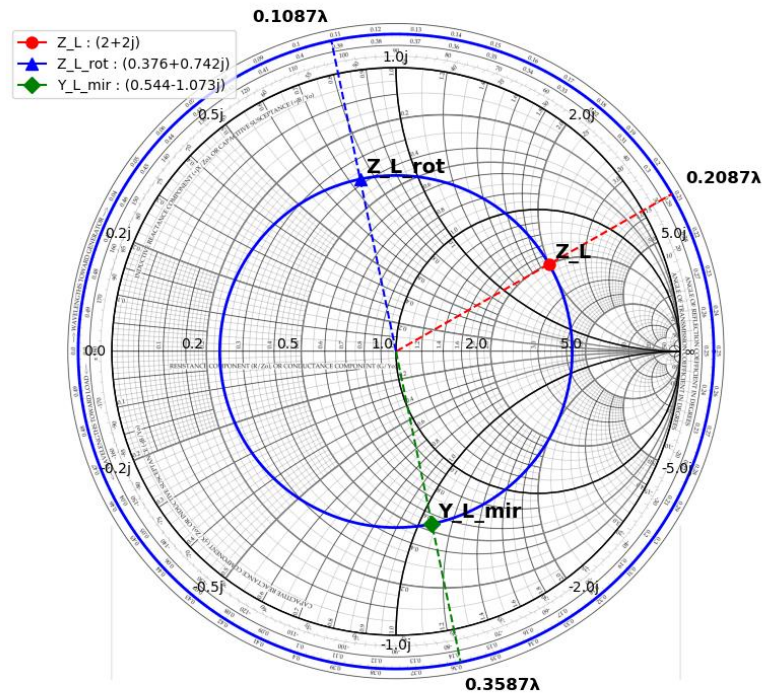



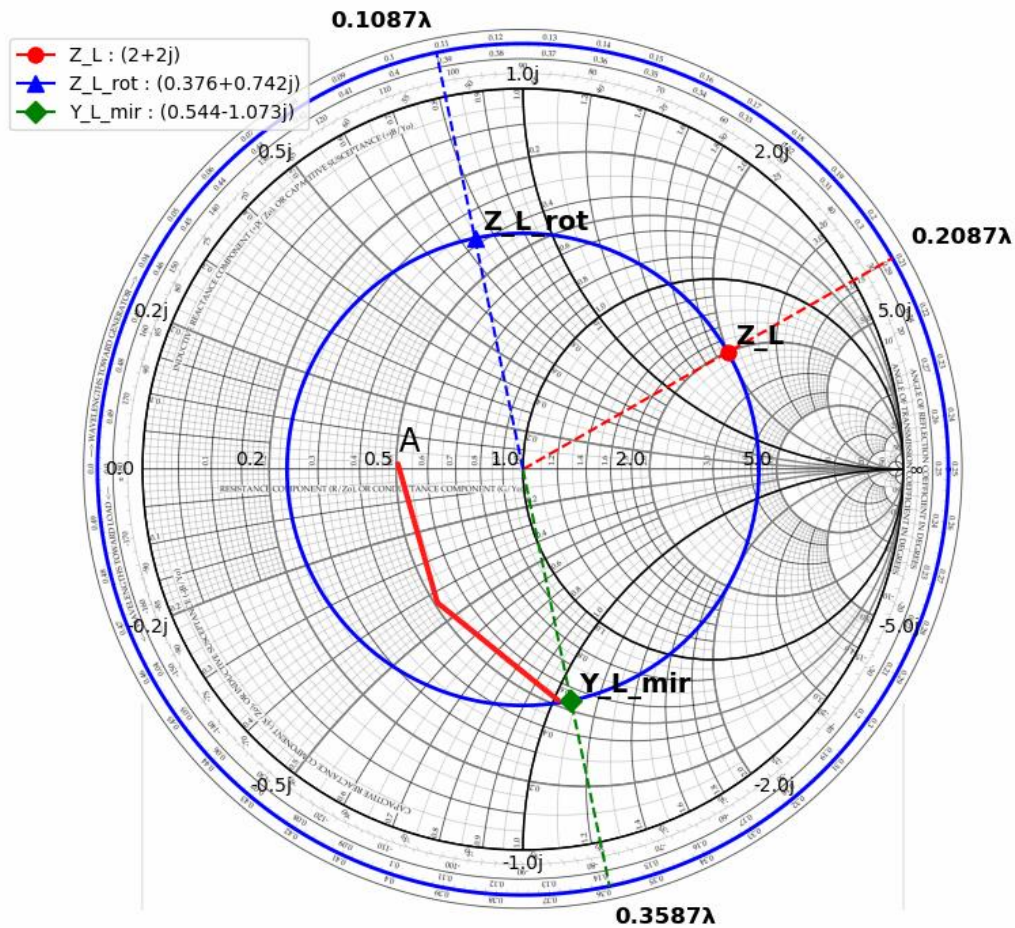
## Steps Six and Seven

The python code does steps 6,7 and 8 automatically. Let's start with step six. From  $Y_{L,mir}$  move along the arc until you have hit the real axis, mark this point as A



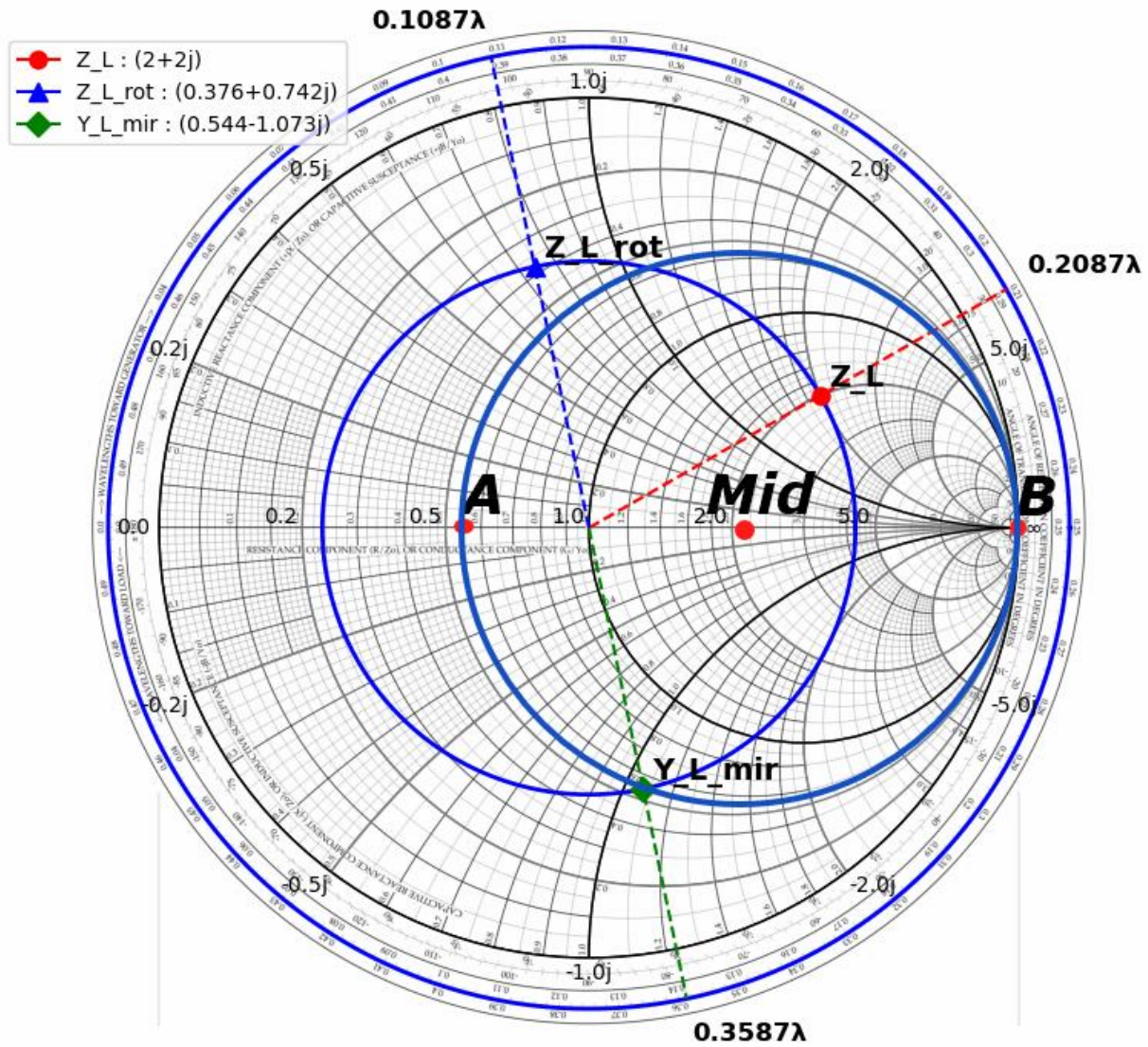For step seven locate the point of infinite conductance, i.e. a short circuit at the right edge of the chart and mark this point as B. from the middle of the road from A to B, draw a radius with length equals to half the distance between A and B.



## Steps Eight

Step eight:

Locate the unity circle of  $1 + Aj$  and rotate it a distance  $d_2$  towards the load, rotation towards the load is counter clockwise. This is done by inserting  $d_2 > 0$ . Mark the two intersection points of the circles as  $Y_{int1}$  and  $Y_{int2}$ .

At this point I highly recommend clearing the chart using remove circle or remove points. It is also possible to open a new chart and directly click on option 4 to continue from the same place.

0. Open a New Chart
New Chart

☒ Short Circuit Mode
☐ Z Mode

1. Enter Load Impedance ( $Z = R + jX$ ):  
R: 2 X: 2 Plot Impedance

2. Enter Rotation Distance:  
d1: -0.4 Rotate d1

3. Mirror  $\Gamma$ : Mirror

4. Enter the distance between the stubs:  
d2 > 0: 0.375 Rotate d2


5. Subtract For L1: Subtract

6. Rotate Unity Back: Rotate Back

7. Clear a Point: Clear Point

8. Clear a Circle: Clear Circle

9. Clear an Arc: Clear Arc

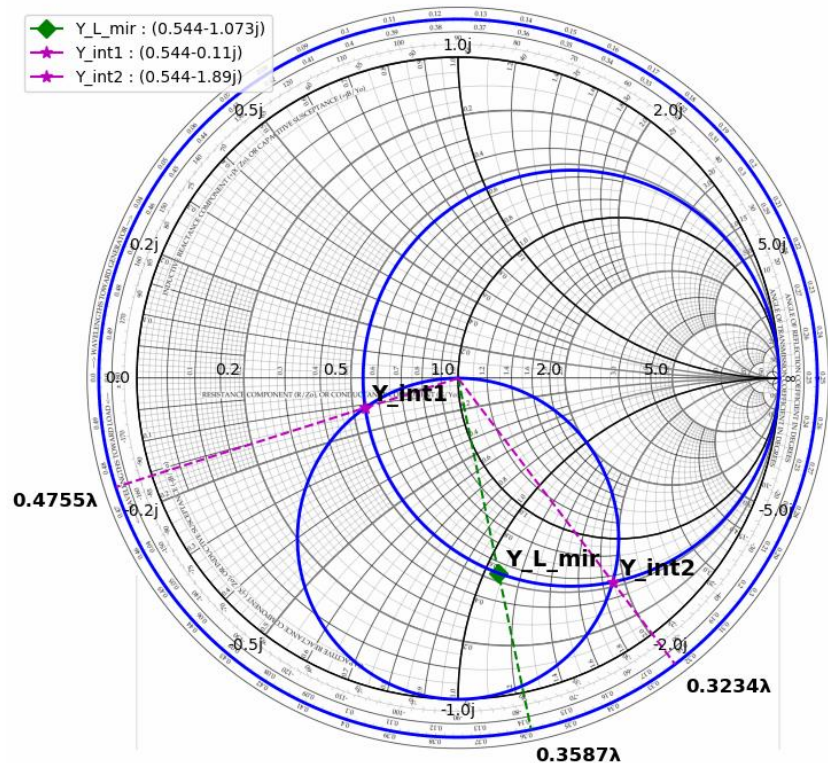

Write down the intersection points they will be needed for later use.

$$Y_{int1} = 0.544 - 0.11j$$

$$Y_{int2} = 0.544 + 1.89j$$



## Steps Nine and Ten

For step nine and ten find the difference between  $Y_{dif} = Y_{L,rot} - Y_{int}$ . Since they are on the same circle the result should be purely imaginary.

Find the point on the chart with the value  $Y_{dif}$ , the clockwise arc from point B to  $Y_{dif}$  is the length of the short circuit stub. This is the length of the first stub.

tk

0. Open a New Chart New Chart

☒ Short Circuit Mode ☐ Z Mode

1. Enter Load Impedance ( $Z = R + jX$ ):

R:  X:  Plot Impedance

2. Enter Rotation Distance:

d1:  Rotate d1

3. Mirror  $\Gamma$ : Mirror

4. Enter the distance between the stubs:

d2 > 0:  Rotate d2


5. Subtract For L1: Subtract

6. Rotate Unity Back: Rotate Back

7. Clear a Point: Clear Point

8. Clear a Circle: Clear Circle

9. Clear an Arc: Clear Arc

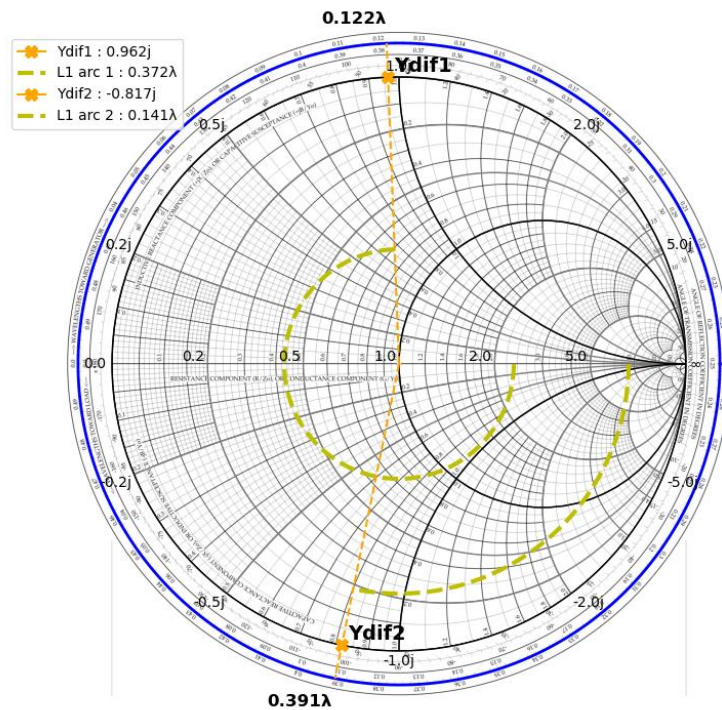

$$Y_{dif1} = 0.962j \Rightarrow L_1 = 0.372\lambda$$

$$Y_{dif2} = -0.817j \Rightarrow L_1 = 0.141\lambda$$



## Steps Eleven and Twelve

For the two last steps rotate the unity circle with the two intersection points  $Y_{int}$  back to its original place. Finally the negative of the imaginary of the rotated points on the chart.

The clockwise arc from point B, on the right edge, to this value is the length of the second stub.

tk

0. Open a New Chart

New Chart

☒ Short Circuit Mode
 ☐ Z Mode

1. Enter Load Impedance ( $Z = R + jX$ ):

$R_L$ : 2

$X_L$ : 2

Plot Impedance

2. Enter Rotation Distance:

$d1$ : -0.4

Rotate  $d1$

3. Mirror  $\Gamma$ :

Mirror

4. Enter the distance between the stubs:

$d2 > 0$ : 0.375

Rotate  $d2$

5. Subtract For  $L1$ :

Subtract

6. Rotate Unity Back:

Rotate Back

7. Clear a Point:


Clear Point

8. Clear a Circle:

Clear Circle

9. Clear an Arc:

Clear Arc

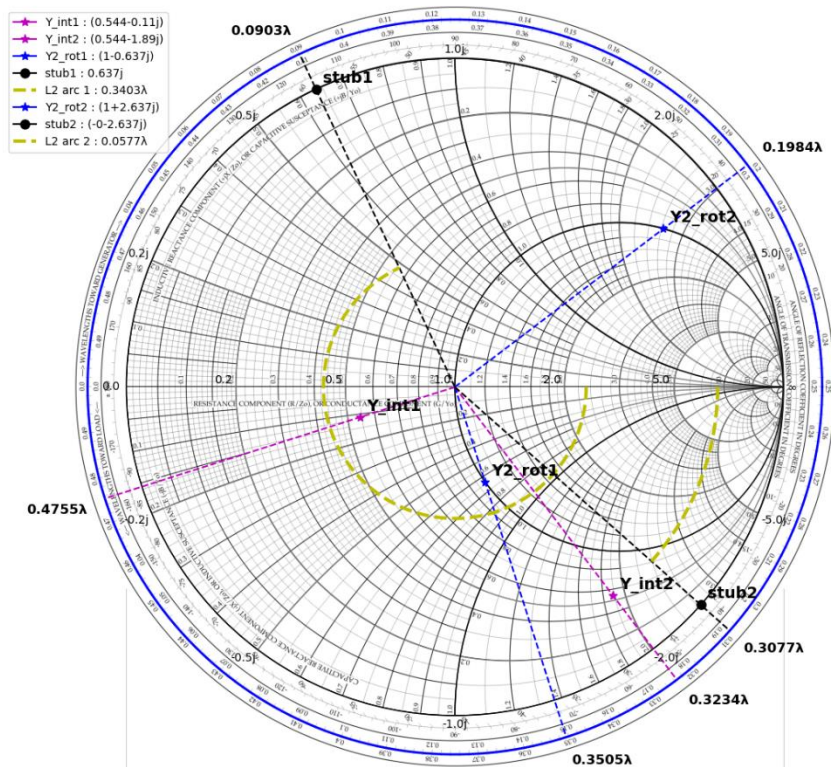

$$L_2 = 0.34\lambda \text{ or } 0.0577\lambda$$

And that's it. Another note is that sometimes matching with the two stubs isn't possible.

Usually, it's when the points land inside the  $2 + Bj$  circle, when in admittance mode.

That means there is no combination of short circuits that will get us to a match.